



OBJECTIVE: Using the Arduino, launch the fan when light is detected.

Parts List

Quantity	ID	Name	Part #
1		Base Grid Base Grid (11 x 7.7)	6SCBG
5	2	2-snap wire	6SC02
1	4	4-snap wire	6SC04
1	7	7-snap wire	6SC07
	R4	10K Ω Resistor	6SCR4
	S1	Slide Switch	6SCS1
	RP	Photo Resistor	6SCRP
1	S3	Relay	6SCS3
1	B1	Battery Holder	6SCB1
2		AA Batteries	
5		Snap-to-Pin wire (red, 2x black, yellow and green)	SCJW10

Step by Step Guide

- 1) Snap the component **B1** between **E10** and **G10** placing the positive (+) terminal on E10.
- 2) Snap the component **S3** between **E6**, **E8**, **G6** and **G8** oriented as shown in the diagram.
- 3) Snap the component **M1** between **D8** and **D10** with the positive (+) terminal on **D8**.
- 4) Snap the component **S1** between **G8** and **G10**. Slide the switch to the "off" position
- 5) Snap the component **RP** between **A2** and **A4**.
- 6) Snap the component **R4** between **A1** and **C1**.
- 7) Connect the snap end of a **red** wire onto the component at position **B3**.
- 8) Snap the 7-snap wire between **A5** and **G5**.
- 9) Snap the 4-snap wire between **A6** and **D6**.

Step by Step Guide

- 10) Snap the 2-snap wire between **D10** and **E10**.
- 11) Snap the 2-snap wire between **D8** and **E8**.
- 12) Snap the 2-snap wire between **D6** and **E6**.
- 13) Snap the 2-snap wire between **G5** and **G6**.
- 14) Snap the 2-snap wire between **A1** and **A2**.
- 15) Connect the snap end of the **green** wire at position **A6**.
- 16) Plug the male pin end of the **green** wire from step 21 into the **D2** pin on the Arduino Uno board
- 17) Connect the snap end of the first **black** wire at position **A5**.
- 18) Plug the male pin end of the **black** wire from step 22 into the **GND** pin on the Arduino Uno board.
- 19) Connect the snap end of the **red** wire at position **A4**.
- 20) Plug the male pin end of the **red** wire from step 25 into the **3V3** pin on the Arduino Uno board.
- 21) Connect the snap end of the first **yellow** wire at position **A1**.
- 22) Plug the male pin end of the **yellow** wire from step 27 into the **D3** pin on the Arduino Uno board.
- 23) Connect the snap end of the second **black** wire at position **C1**.
- 24) Plug the male pin end of the **black** wire from step 29 into the **GND** pin on the Arduino Uno board.
- 25) Download the Arduino sketch to your Arduino Uno board
- 26) Insert the AA batteries into component **B1** paying attention to proper polarity.

Step by Step Guide (continued)

27. Slide the switch **S1** into the “on” position.
28. Place the fan onto the motor **M1** making sure the grooves rest properly on the top.
29. Press and hold the button **S2** on the circuit to start the motor.
30. Release the button to launch the fan.
31. Place the fan back onto the motor and press the button again.
32. Repeat as many times as you like.

Notes

1. If the fan does not launch when the motor turns off check the placement. If it still does not launch check that you have fresh AA batteries.