
Daniel Porrey
Snap Circuits IoT
https://www.hackster.io/porrey

## **Internet Music**

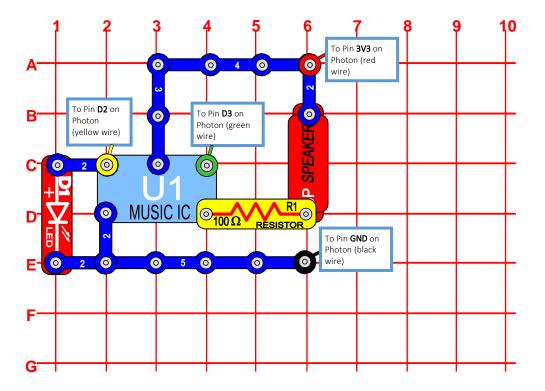

OBJECTIVE: To show how to use a Photon and Tinker to turn trigger music from your smartphone.

## **Parts List**

Quantity	ID	Name	Part #
1		Base Grid Base Grid (11 x 7.7)	6SCBG
4		1-snap wire	6SC01
1		2-snap wire	6SC02
1		3-snap wire	6SC03
1		4-snap wire	6SC04
1		5-snap wire	6SC05
1	D1	Red LED	6SCD1
1	R1	100 Ω Resistor	6SCR1
1	SP	Speaker	6SCSP
1	U1	Music IC	6SCU1
4		Snap-to-Pin wire (red, black, green and yellow)	SCJW10

## **Step by Step Guide**

- 1) Snap component **D1** between **C1** and **E1**
- 2) Snap the four corners of the component **U1** at **C2**, **D2**, **C4** and **D4** (see diagram for correct orientation)
- 3) Snap component SP between B6 and D6
- 4) Connect a 4 snap wire between A3 and A6
- 5) Connect a 5 snap wire between **E2** and **E6**
- 6) Snap component **R1** over the components at **D4** and **D6**
- 7) Connect a 2 snap wire over the components at **E2** and **D2**
- 8) Connect a 1 snap wire over the component at **E1**
- 9) Connect a 2 snap wire over the components at **E1** and **E2**
- 10) Connect a 2 snap wire over the components at C1 and C2
- 11) Connect a 3 snap wire over the components at A3 and C3
- 12) Connect a 2 snap wire over the components at **A6** and **B6**
- 13) Connect the snap end of a **black** wire onto the component at position **E6**

## **Step by Step Guide** (continued)

- 14) Plug the bread board end of the **black** wire from step 13 into **GND** on the Photon in the breadboard
- 15) Connect the snap end of a **red** wire onto the component at position **A6**
- 16) Plug the bread board end of the **red** wire from step 15 into **3V3** on the Photon in the breadboard
- 17) Connect the snap end of a **green** wire onto the component at position **C4**
- 18) Plug the bread board end of the **green** wire from step 17 into **D3** on the Photon in the breadboard
- 19) Connect the snap end of a **yellow** wire onto the component at position **C2**
- 20) Plug the bread board end of the **yellow** wire from step 19 into **D2** on the Photon in the breadboard
- 21) Connect your Photon to your power source
- 22) Open the Tinker application on your smartphone
- 23) Choose Get Started and select your Photon board in the UI
- 24) Click the **D2** button and select **digitalWrite**
- 25) Click the **D2** button to set the pin to HIGH. Music will play once and the LED will stay lit until your set this pin back to LOW
- 26) Click the **D3** button and select **digitalWrite**
- 27) Click the **D3** button to set the pin to HIGH. Music will until your set this pin back to LOW