
Daniel Porrey
Snap Circuits IoT
https://www.hackster.io/porrey

## **Internet Sounds**

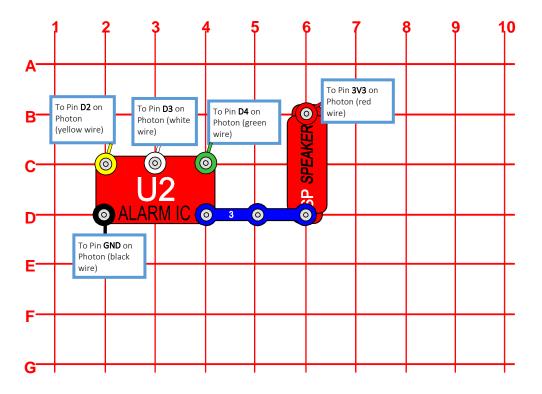

OBJECTIVE: To show how to use a Photon and Tinker to turn trigger different sounds from your smartphone.

## **Parts List**

Quantity	ID	Name	Part #
1		Base Grid Base Grid (11 x 7.7)	6SCBG
1		3-snap wire	6SC03
1	SP	Speaker	6SCSP
1	U2	Alarm IC	6SCU2
5		Snap-to-Pin wire (red, black, green, white and yellow)	SCJW10

## **Step by Step Guide**

- 1) Snap the four corners of the component **U1** at **C2**, **D2**, **C4** and **D4** (see diagram for correct orientation)
- 2) Snap component SP between B6 and D6
- 3) Connect a 3 snap wire between **D4** and **D6**
- 4) Connect the snap end of a **black** wire onto the component at position **D2**
- 5) Plug the bread board end of the **black** wire from step 4 into **GND** on the Photon in the breadboard
- 6) Connect the snap end of a **yellow** wire onto the component at position **C2**
- 7) Plug the bread board end of the yellow wire from step 6 into pin **D2** on the Photon in the breadboard
- 8) Connect the snap end of a **white** wire onto the component at position **C3**
- 9) Plug the bread board end of the white wire from step 8 into pin **D3** on the Photon in the breadboard
- 10) Connect the snap end of a **green** wire onto the component at position **C4**
- 11) Plug the bread board end of the **white** wire from step 10 into pin **D4** on the Photon in the breadboard
- 12) Connect your Photon to your power source

## Step by Step Guide (continued) 14) Choose Get Started and select your Photon board in the UI 15) Open the Tinker application on your smartphone 16) Click the D2 button and select digitalWrite 17) Click the D3 button and select digitalWrite 18) Click the D4 button and select digitalWrite 19) No vary the three pins, D2, D3 and D4 between HIGH and LOW to create different sounds