



OBJECTIVE: This experiment will demonstrate how the Snapduino can control an analog motor using an SCR.

Parts List

| Quantity | ID | Name | Part # |
|----------|----|----------------------------------|--------|
| 1 | | Base Grid Base Grid (11" x 7.7") | 6SCBG |
| 2 | 1 | 1-snap wire | 6SC01 |
| 2 | 2 | 2-snap wire | 6SC02 |
| 1 | UA | Snapduino | |
| 1 | | Snap-FTDI Cable | |
| 1 | R1 | 100 Ω Resistor | 6SCR1 |
| 1 | D3 | Diode 1N4001 | 6SCD3 |
| 1 | S1 | Slide Switch | 6SCS1 |
| 1 | M1 | Motor | 6SCM1 |
| 1 | Q3 | SCR | 6SCQ3 |
| 1 | B1 | Battery Holder | 6SCB1 |
| 1 | | Jumper Wire (Black) | 6SCI1 |

Step by Step Guide

- 1) Place the upper-left corner of the Snapduino at **C1**.
- 2) Snap component **Q3** between position **D5**, **C6** and **E6**.
- 3) Snap a 1-snap wire on the component at **B6**.
- 4) Snap a 1-snap wire on the component at **B8**.
- 5) Snap component **D3** between position **B6** and **B8**.
- 6) Snap component **B1** between position **C8** and **E8**.
- 7) Snap component **R1** over the components between position **D3** and **D5**.
- 8) Snap component **M1** over the components between position **C6** and **C8**.
- 9) Snap component **S1** over the components between position **E6** and **E8**.
- 10) Snap a 2-snap wire over the components between **B6** and **C6**.
- 11) Snap a 2-snap wire over the components between **B8** and **C8**.

- 12) Connect the black jumper wire over the components between **E1** and **E8**.
- 13) Connect the **black** lead of the FTDI cable to the **GND** snap marked with a black ring on the Snapduino (*snap it over the top of any components that may already be connected to this snap*).
- 14) Connect the **green** lead of the FTDI cable to the **Reset** snap marked with a green ring on the Snapduino (*snap it over the top of any components that may already be connected to this snap*).
- 15) Connect the **yellow** lead of the FTDI cable to the **PB0** snap marked with a yellow ring on the Snapduino (*snap it over the top of any components that may already be connected to this snap*).
- 16) Connect the **white** lead of the FTDI cable to the **PB1** snap marked with a white ring on the Snapduino (*snap it over the top of any components that may already be connected to this snap*).
- 17) Connect the **red** lead of the FTDI cable to the **5V** snap marked with a red ring on the Snapduino (*snap it over the top of any components that may already be connected to this snap*).
- 18) Open the sketch for this project in the Arduino IDE and upload it to the board.
- 19) Place two fresh AA batteries into the battery holder.
- 20) When the upload has completed, Place the switch **S1** in the ON position.
- 21) The motor will run for 3 seconds and then stop for 3 seconds. This will repeat while the Snapduino is powered and the switch **S1** is in the ON position.

